

CONTINUOUS INTERNAL EVALUATION- 3

Dept:EC	Sem / Div:IV B	Sub:Analog Circuits	S Code:18EC42
Date:22/07/2021	Time: 2:00-3:30 pm	Max Marks: 50	Elective:N
Note: Answer any 2 full questions, choosing one full question from each part.			

Q N	Questions	Marks	RBT	COs
PART A				
1	a How does negative feedback affect the performances of an inverting amplifier using opamp? Derive the relevant expressions for Gain, input resistance and output resistance	8	L2	CO4
	b Explain the operation of 4-bit Binary weighted DAC with neat circuit. For the Binary weighted DAC, with $R=10k\Omega$ and $R_F=1k\Omega$ and $V_{REF}=5V$, determine the output voltage when the inputs $b_0=b_2=0V$ and $b_1=b_3=5V$	8	L3	CO4
	c What is an instrumentation amplifier? What are its applications? With a neat circuit diagram explain an instrumentation amplifier using a transducer bridge.	9	L2	CO4
2	a Draw the circuit and waveforms for an inverting Schmitt Trigger using opamp, with relevant expressions.	10	L2	CO4
	b Draw the circuit of second order high pass filter and explain its operation.	9	L2	CO4
	c For an opamp non-inverting amplifier using 741 IC with $R_L=1 K\Omega$ and $R_F=10K\Omega$, $A= 200,000$; $R_i=2M\Omega$, $R_o = 75\Omega$, $f_o =5 Hz$; supply voltages $\pm 15V$, output voltage swing = $\pm 13V$, Compute A_F , R_{if} , R_{of} , f_{f} .	6	L3	CO4
3	a Explain summing, scaling and averaging amplifier in inverting configuration	8	L2	CO4
	b Draw the circuit and frequency response of a first order low pass filter. Design a first order low pass filter to have a cutoff frequency of 1kHz with a passband gain of 2.	10	L3	CO4
	c Explain the R-2R DAC with a neat sketch.	7	L2	CO4
4	a The opamp 714C is connected as an inverting amplifier with $R_1=1k\Omega$ and $R_F=4.7k\Omega$. Compute the closed loop parameters: A_F , R_{IF} , R_{OF} , f_F . . Given $A=400000$, $R_i=33M\Omega$ and $R_O=60\Omega$; supply voltages are $\pm 13V$; Max output voltage swing = $\pm 13V$, Unity gain bandwidth = $0.6MHz$.	10	L3	CO4
	b Explain the working of a Successive Approximation type of ADC.	9	L2	CO4
	c Explain with a neat circuit diagram, the working of a positive small signal half wave precision rectifier using an Opamp.	6	L2	CO4